

# **DIGITAL SYSTEM DESIGN USING VERILOG**

- **Course code:** 18EC5DCDSV
- **Credits:** 03

### **Course Objectives:**

- To study Verilog HDL in high-level synthesis of digital system designs.
- To learn Verilog HDL for modelling, simulating and synthesizing various digital modules.
- To study the additional features of Verilog HDL
- To be able to design and develop Test bench for Combinational and sequential modules
- To be able to design fixed and floating point arithmetic
- To be able to design and implement synchronous sequential circuits using FSM

# Course Outcomes

CO1	Describe & model digital blocks of computing systems using Verilog hardware description language..
CO2	Apply hardware description language for writing test benches to check combinational & sequential modules.
CO3	Design clocked synchronous circuits and perform timing analysis
CO4	Analyze digital System and model using Verilog HDL.
CO5	Apply design Knowledge to FSM based digital Modules.
CO6	Synthesize and implement a given digital system.

# Module 1

- **Computer-Aided Design , Hardware Description Languages, Module modelling styles(ming bo lin), Verilog Description of Combinational Circuits,**
- **Data flow modelling-dataflow modelling, operands, operators, (ming bo lin), Verilog Modules, Verilog Assignments, Procedural Assignments), Modeling Flip-Flops Using Always Block, Always Blocks Using Event Control Statements.[Text book 1 and 3] Delays in Verilog, Compilation, Simulation, and Synthesis of Verilog Code , Simple Synthesis Examples**
- **TEXT BOOKS:Charles H Roth Jr., Lizy Kurian John, Byeong –kill-lee “Digital System Design using Verilog”, *publisher Cengage learning***
- **Ming-Bo Lin, “Digital System designs and Practices using Verilog HDL and FPGAs”, *John Wiley & Sons, 2008***

# Introduction to verilog


- Complexity
- Tedious and Time consuming
- Hand drawn Schematics, breadboards and wires
- More and more components on a chip,
- Improvements have advanced the **VLSI** (very large scale integration) field

- **SSI (small-scale integration),**
- **MSI (medium-scale integration),**
- **LSI (large-scale integration)**
- **All depends on the density of integration.**
- **SSI referred to ICs with 1 to 20 gates**
- **MSI referred to ICs with 20 to 200 gates**
- **LSI referred to devices with 200 to a few thousand gates**
- **Building blocks such as adders, multiplexers, decoders, registers, and counters are available as MSI standard parts.**
- **Term VLSI was coined, devices with 10,000 gates were called VLSI chips. The boundaries between the different categories are fuzzy today. Many modern microprocessors contain more than 100 million transistors. Compared to what was referred to as VLSI in its initial days**
- **Modern integration capability could be described as ULSI (ultra large scale integration). Despite the changes in integration ability and the fuzzy definition, the term VLSI remains popular.**

# Computer-aided design


- **(CAD)** tools have advanced significantly during the past decade, and nowadays digital design is performed using a variety of software tools.
- Prototypes or even final designs can be created without discrete components and interconnection wires.
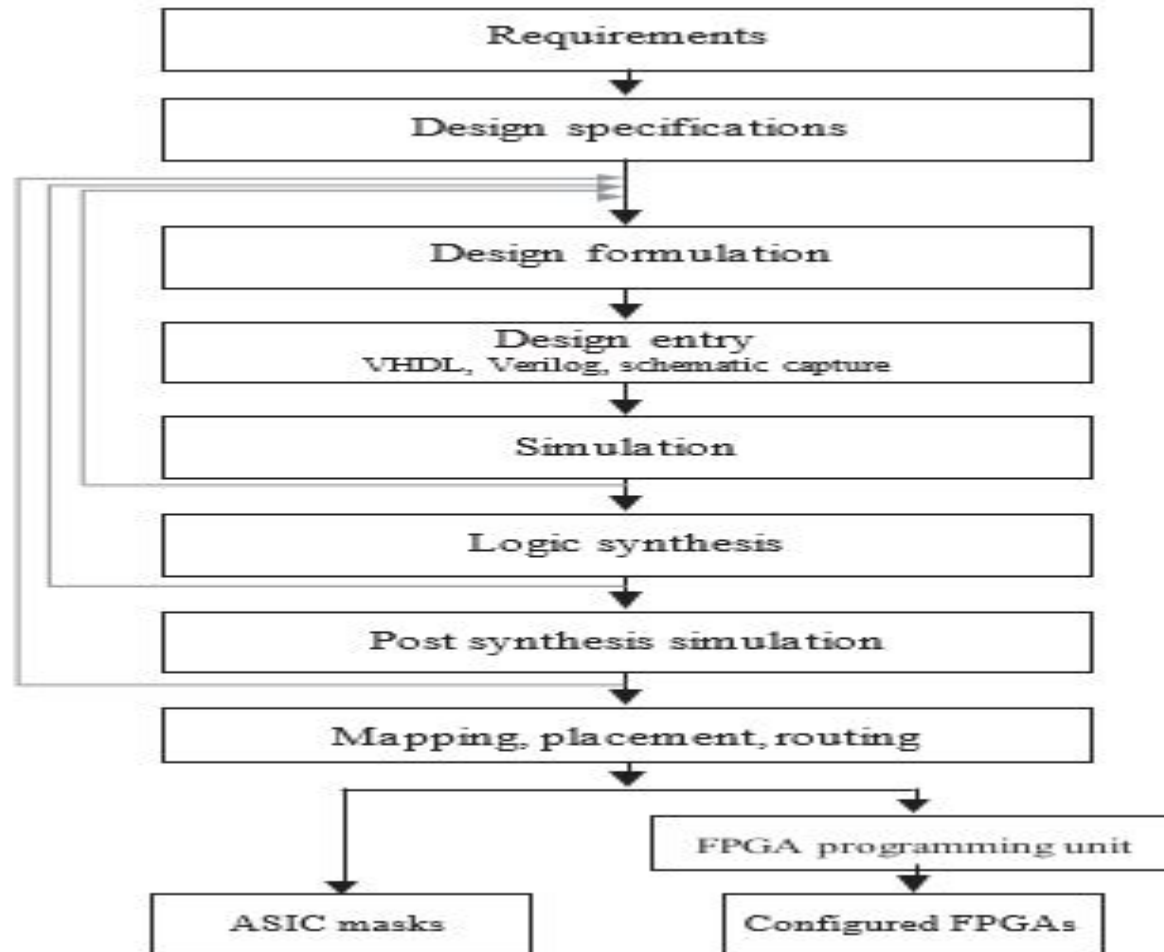
# Design Flow in Modern Digital System Design





# Spectrum of Design Technologies

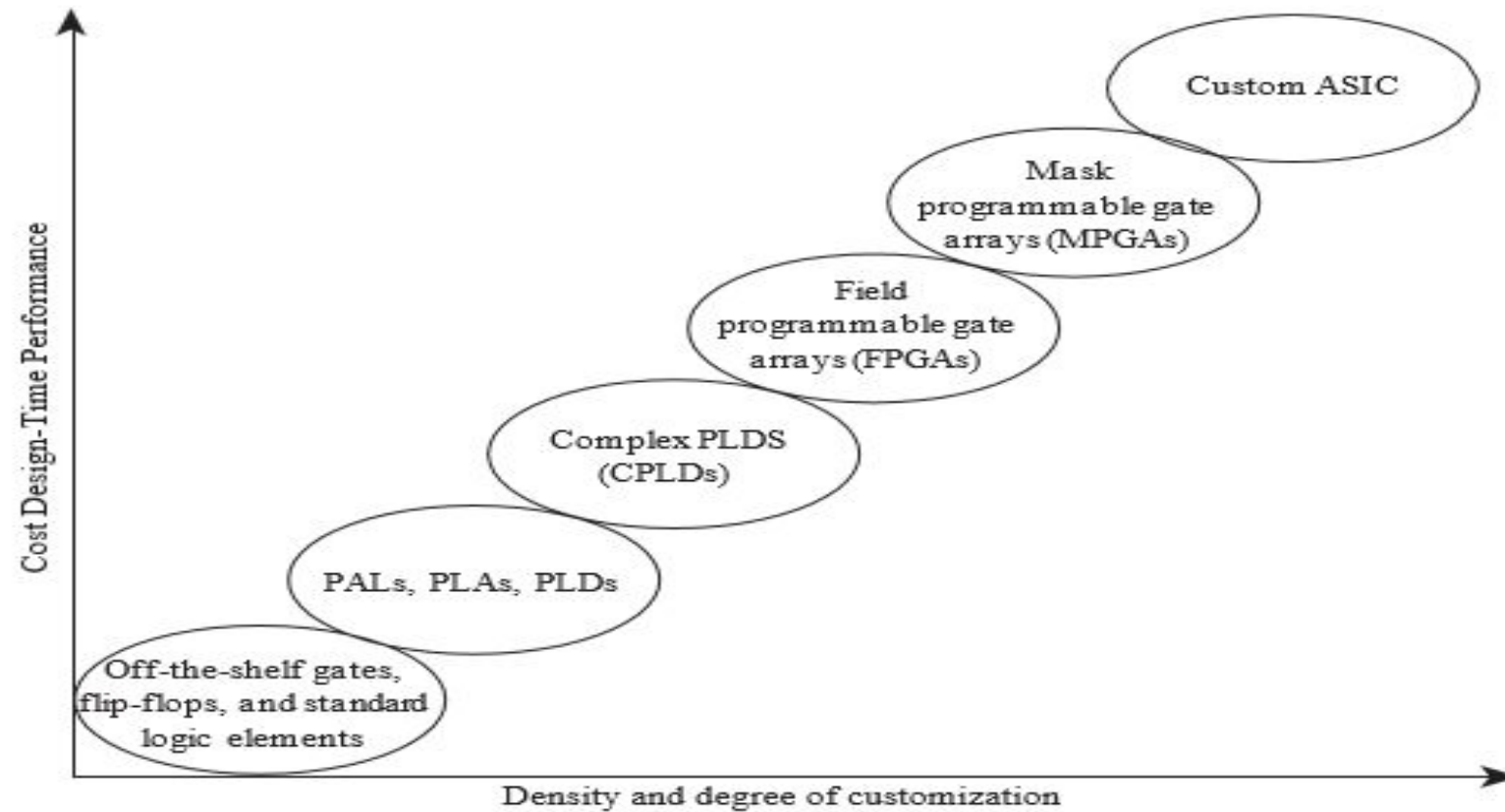

# Hardware Description Languages

- Hardware description languages (HDLs) are a popular mode of design entry for digital circuits and systems.
- There are two popular HDLs—VHDL and Verilog.
- Before the advent of HDLs, designers used graphical schematics and schematic capture tools to document and simulate digital circuits.
- A need was felt to create a textual method of documenting circuits and feeding them into simulators in the textual form as opposed to a graphic form.

# Verilog

- Verilog is a hardware description language used to describe the behavior and/ or structure of digital systems
- Verilog is a general-purpose hardware description language that can be used to describe and simulate the operation of a wide variety of digital systems, ranging in complexity from a few gates to an interconnection of many complex integrated circuits.
- VHDL was originally developed under funding from the Department of Defense (DoD)
- Verilog was developed by the industry. It was initially developed as a proprietary language by a company called Gateway Design Automation around 1984.
- In 1990, Cadence acquired Gateway Design Automation and became the owner of Verilog. Cadence marketed it as a language and as a simulator, but it remained proprietary.
- At this time, Synopsis was promoting the concept of top-down design using Verilog. Cadence realized that it needed to make Verilog open in order to prevent the industry from shifting to VHDL and hence opened up the language.
- An organization called Open Verilog International (OVI) was formed, which helped to create a vendor-independent language specification for Verilog, clarifying many of the confusions around the proprietary specification. This was followed by an effort to create an IEEE standard for Verilog. The first Verilog IEEE Standard was created in 1995, which was revised in 2001 and 2005. Synopsis created synthesis tools for Verilog around 1988

# Module Modelling Styles

- Synthesis is process that converts HDL modules into a structural description
- It is divided into logic synthesis and high level synthesis
- RTL description into gate level netlist
- High level description into RTL results

- MODULES

□ Two parts

- Interface
- Internal

## Modeling the Internal of a Module

- 1.Structural Style
  - Gate Level
  - Switch Level

## 2.Dataflow Style

- Module is specified as a set of continuous assignments statements

## 3.Behavioral or algorithmic style

## 4.Mixed style

- modelling Large Designs

# Port Declaration

- Interface signals of any Verilog HDL module can be of three types

- ☐ Input

- ☐ output

- ☐ Inout

- The complete interface of a module is to divide it into three parts

- ☐ Port list

- ☐ Port Declaration

- ☐ Data type declaration of each type

# Port List style

```
module adder(x,y,c_in,sum,c_out)
```

```
    Input [3:0] x,y;
```

```
    Input c_in;
```

```
    output [3:0] sum;
```

```
    output c_out;
```

```
    reg [3:0] sum;
```

```
    reg c_out;
```

This style of port declaration is known as port list style

```
module adder(x,y,c_in,sum,c_out)
```

```
    Input [3:0] x,y;
```

```
    Input c_in;
```

```
    output reg [3:0] sum ;
```

```
    output reg c_out;
```

```
module adder(input [3:0]x,y, input c_in, output reg [3:0] sum
```

```
    output reg c_out );
```



# Port Connection Rules

- Named association
- Positional association

## *Coding Styles*

- A module cannot be declared within another module
- A module can instantiate other modules
- A module instantiation must have a module identifier (instance name) except built in primitives, gate and switch primitives and user defined primitives

Named association at the top level modules to avoid confusion

# Port connection Rules

```
module half adder(x,y,s,c);
```

```
Input x,y;
```

```
Output ,c;
```

```
//half adder body//
```

```
//instantiate primitive gates
```

```
xor xor1(s,x,y);      ( s,x,y)-Positional association
```

```
and and1 (c,x,y);    and1 (instance name is optional)
```

```
endmodule
```

```
module full_adder(x,y,cin,s,cout);  
Input x,y,cin;  
output s,cout;  
wire s1,c1,c2;  
// full adder body//  
// instantiate the half adder  
half adder ha_1(x,y,s1,c1);      // (x,y,s1,c1)-Positional association  
half adder ha_2(.x(cin), .y(s1), .s(s), .c(c2)); //ha_2(instance name is necessary)  
Or (cout,c1,c2);                //(.x(cin), .y(s1), .s(s), .c(c2))-Named association  
endmodule
```


# Structural Modelling


- Structural Modelling at gate level

The Half adder instantiates two gate primitives

The Full adder instantiates two half modules and one gate primitive

 The Four bit adder is constructed by four full adders instances



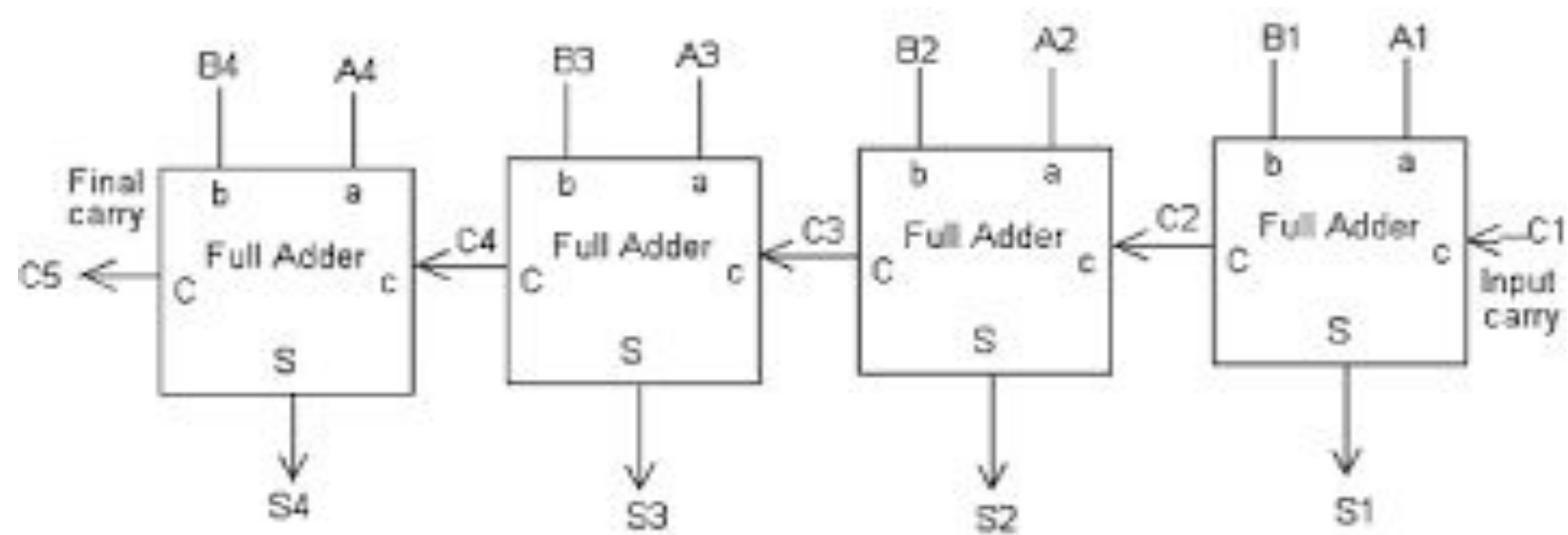

# Gate level description of half adder

```
module half adder(x,y,s,c);  
  Input x,y;  
  Output s,c;  
  //half adder body  
  // instantiate primitive gates  
  xor(s,x,y);  
  and(c,x,y);  
endmodule
```

# Gate level description of Full adder

```
module full adder(x,y,cin,s,cout);  
input x,y ,cin;  
output s,cout;  
Wire s1,c1,c2;  
//full adder body  
//instantiate the half adder  
half _adder ha_1(x,y,s1,c1);  
half_adder ha_2(cin,s1,s,c2);  
Or(cout,c1,c2);  
endmodule
```



# Gate level description of 4 bit adder

```
module 4_bit_adder(x,y,c_in,sum,c_out);  
Input [3:0] x,y;  
Input c_in;  
output [3:0] sum;  
output c_out;  
Wire c1,c2,c3;  
//4_bit adder body  
// instantiate the full adder
```

```
full_adder fa_1(x[0],y[0],c_in,sum[0],c1);  
full_adder fa_2 (x[1],y[1],c1,sum[1],c2);  
full _adder fa_3(x[2],y[2],c2,sum[2],c3);  
full _adder fa_4(x[3],y[3],c3,sum[3],c_out);  
endmodule
```

# Dataflow Modelling

- Continuous assignment
- Keyword used "assign"

syntax

`assign[delay] 1_value=expression;`

- ✓ Expression is evaluated and result is assigned to 1\_value after the specified delay
- ✓ Default –zero delay

```
module full_adder_dataflow(x,y,c_in,sum,c_out);  
// I/O port declarations  
Input x,y,c_in;  
output sum,c_out;  
//specify the function of full adder  
  
assign #5 {c_out,sum} =x+y+c_in;  
endmodule
```

# Behavioral Modelling

- Two procedural constructs

- Initial


- Always

Initial statement used to set up initial values of variable data types

Always are used to model combinational and sequential logic

```
module full_adder_behavioral(x,y,c_in,sum,c_out);  
Input x,y,c_in;  
output sum,c_out;  
reg sum,c_out;  
always @(x,y,c_in)  
#5 {c-out,sum}=x+y+c_in;  
endmodule
```

# Verilog program structure

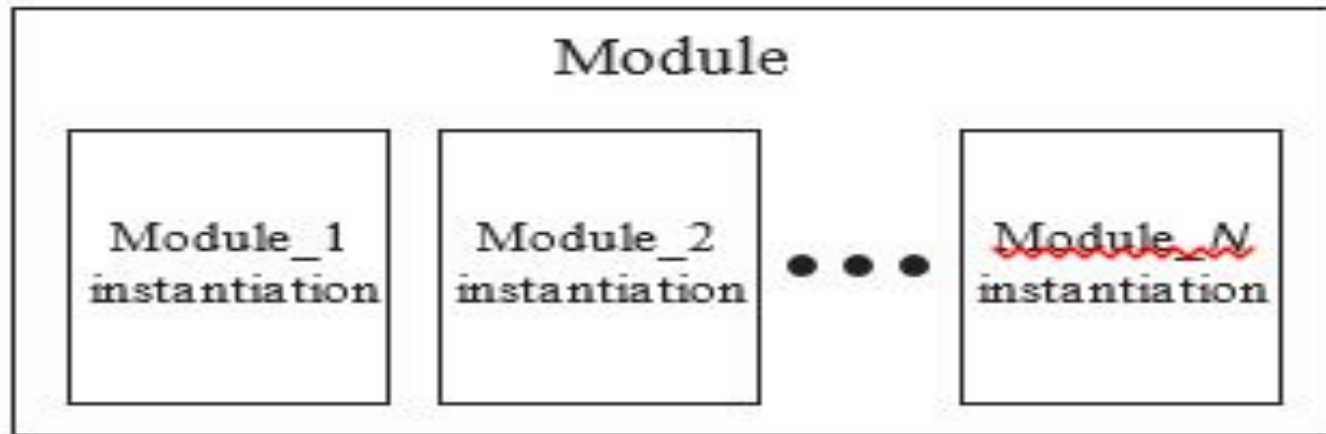

Each module declaration includes a list of interface signals that can be used to connect to other modules or to the outside world.

# Module Declaration

```
module module-name (module interface list);  
[list-of-interface-ports]  
...  
[port-declarations]  
...  
[functional-specification-of-module]  
...  
endmodule
```



The items enclosed in square brackets are optional. The list-of-interface- ports normally has the following form:


**type-of-port list-of-interface-signals**

**{; type-of-port list-of-interface-signals};**

- The curly brackets indicate zero or more repetitions of the enclosed clause. Type-of-port indicates the direction of information; whether information is flowing into the port or out of it.
- Input port signals are of keyword **input**, output port signals are of keyword **output**, and bidirectional signals are of keyword **inout**. Also, list-of- ports can be combined with the module interface list.

 
# Verilog Modules

- The general structure of a Verilog code is a module description.
- A module is a basic building block that declares the input and output signals and specifies the internal operation of the module
- The **module** declaration has the name `two_gates` and specifies the inputs and outputs. *A*, *B*, and *D* are input signals, and *E* is an output signal.
- The signal *C* is declared within the module as a **wire** since it is an internal signal.
- The two concurrent statements that describe the gates are placed and the module ends with **endmodule**. All the input and output signals are listed in the module statement without specifying whether they are input or output.



```
module two_gates (A, B, D, E);  
output E;  
  
input A, B, D;  
  
wire C;  
  
    assign C = A && B; // concurrent  
    assign E = C || D; // statements  
endmodule
```

# Multiplexer Design

 

Sel[1:0]	mux_out
00	i0
01	i1
10	i2
11	i3

- A multiplexer of  $2^n$  inputs has  $n$  select lines, are used to select which input line to send to the output.
- There is only one output in the multiplexer
- Simple 4: 1 Multiplexer with a registered output
- Based on the select input Sel[1:0], mux\_out shall be any one of  $i_0, i_1, i_2, i_3$  as shown in truth table above
- Multiplexer output is registered in the last stage

**module** <module Name> (ports);


Inputs, outputs, inout ports; parameters

Assign statements (concurrent)

Initial statements (procedural)

Always statements (procedural)

**endmodule**

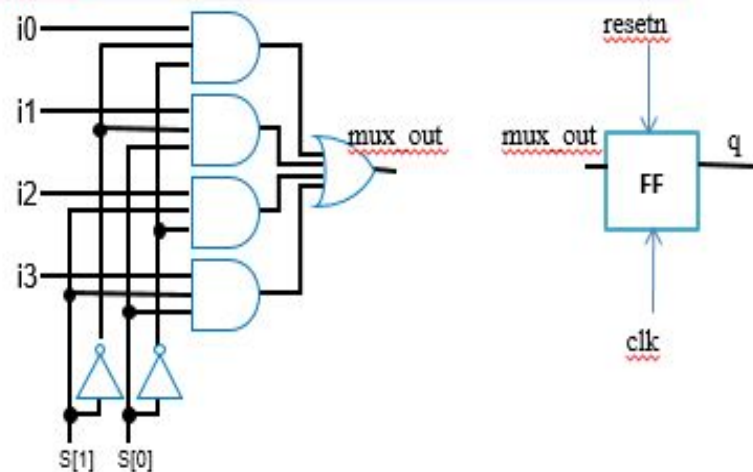

// Multiplexer in Data flow model

**module** mux\_ex (i0, i1, i2, i3, clk, resetn, sel, q);

**input** clk, resetn;

**input** i0, i1, i2, i3;

**input** [1:0] sel;

**output** q;

**reg** q\_out;

**wire** mux\_out;

// concurrent assignments

**assign** mux\_out = sel[1] ? ( sel[0] ? i3 : i2 ) : ( sel[0] ? i1 : i0 );

**always** @(posedge clk or resetn)

**begin**

**if** (!resetn)

q\_out <= 0;

**else**

q\_out <= mux\_out;

**end**

**assign** q = q\_out;

**endmodule**

ports

Module

Module I/Os

Wire, reg  
declarations

Concurrent  
assignments

Procedural block

Sensitivity list

Sequential  
statements

End module

**module** <module Name> (ports);

Inputs, outputs, Inout ports; parameters

Assign statements (concurrent)

Initial statements (procedural)

Always statements (procedural)

**endmodule**

// Multiplexer in Data flow model

**module** mux\_ex ( i0, i1, i2,i3,clk, resetn, sel,q);

**input** clk, resetn;

**input** i0, i1,i2,i3;

**input** [1:0] sel;

**output** q;

**reg** q\_out;

**wire** mux\_out;

// concurrent assignments

**assign** mux\_out = sel[1] ? ( sel[0] ? i3: i2) : ( sel[0] ? i1: i0);

**always** @(posedge clk or resetn)

**begin**

**if** (!resetn)

q\_out <= 0;

**else**

q\_out <= mux\_out;

**end**

**assign** q = q\_out;

**endmodule**