

Port Connection Rules

- Named association
- Positional association

Coding Styles

- A module cannot be declared within another module
- A module can instantiate other modules
- A module instantiation must have a module identifier (instance name) except built in primitives, gate and switch primitives and user defined primitives

Named association at the top level modules to avoid confusion

Structural Modelling

- Structural Modelling at gate level

The Half adder instantiates two gate primitives

The Full adder instantiates two half modules and one gate primitive


The Four bit adder is constructed by four full adders instances



You



Verilog program structure

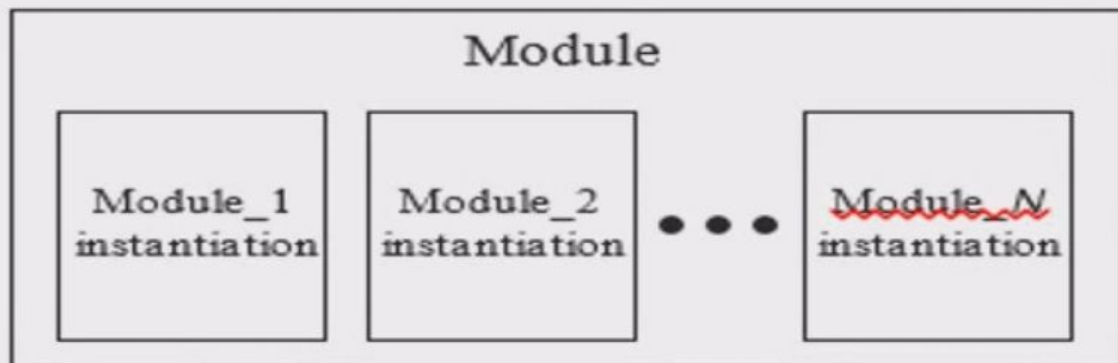

Each module declaration includes a list of interface signals that can be used to connect to other modules or to the outside world.



You



Module Declaration

```
module module-name (module interface list);  
[list-of-interface-ports]  
...  
[port-declarations]  
...  
[functional-specification-of-module]  
...  
endmodule
```



You



The items enclosed in square brackets are optional. The list-of-interface- ports normally has the following form:

type-of-port list-of-interface-signals

{; type-of-port list-of-interface-signals};

- The curly brackets indicate zero or more repetitions of the enclosed clause. Type-of-port indicates the direction of information; whether information is flowing into the port or out of it.
- Input port signals are of keyword **input**, output port signals are of keyword **output**, and bidirectional signals are of keyword **inout**. list-of- ports can be combined with the module interface list.




You



Verilog Modules

- The general structure of a Verilog code is a module description.
- A module is a basic building block that declares the input and output signals and specifies the internal operation of the module
- The **module** declaration has the name `two_gates` and specifies the inputs and outputs. *A*, *B*, and *D* are input signals, and *E* is an output signal.
- The signal *C* is declared within the module as a **wire** since it is an internal signal.
- The two concurrent statements that describe the gates are placed and the module ends with **endmodule**. All the input and output signals are listed in the module statement without specifying whether they are input or output.

 



```
module two_gates (A, B, D, E);  
  output E;  
  
  input A, B, D;  
  
  wire C;  
  
  assign C = A && B; // concurrent  
  assign E = C || D; // statements  
endmodule
```



You



Multiplexer Design

  

| Sel[1:0] | mux_out |
|----------|---------|
| 00 | i_0 |
| 01 | i_1 |
| 10 | i_2 |
| 11 | i_3 |

- A multiplexer of 2^n inputs has n select lines, are used to select which input line to send to the output.
- There is only one output in the multiplexer
- Simple 4: 1 Multiplexer with a registered output
- Based on the select input Sel[1:0], mux_out shall be any one of i_0, i_1, i_2, i_3 as shown in truth



You



```
module <module Name> (ports);
```


Inputs, outputs, inout ports; parameters

Assign statements (concurrent)

Initial statements (procedural)

Always statements (procedural)

```
endmodule
```

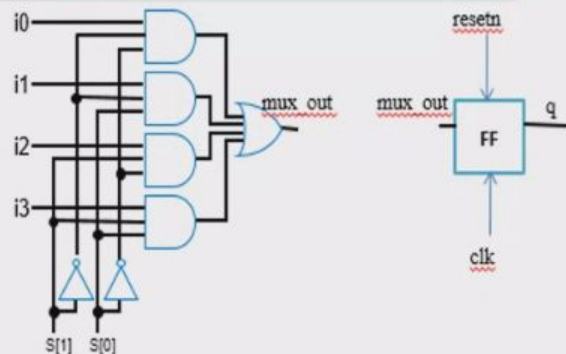

```
// Multiplexer in Data flow model
```

```
module mux_ex (i0, i1, i2, i3, clk, resetn, sel, q);
```

```
input clk, resetn;
```

```
input i0, i1, i2, i3;
```

```
input [1:0] sel;
```

```
output q;
```

```
reg q_out;
```

```
wire mux_out;
```

```
// concurrent assignments
```

```
assign mux_out = sel[1] ? ( sel[0] ? i3: i2) : ( sel[0] ? i1: i0);
```

```
always @(posedge clk or resetn)
```

```
begin
```

```
if (!resetn)
```

```
q_out <= 0;
```

```
else
```

```
q_out <= mux_out;
```

```
end
```

```
assign q = q_out;
```

```
endmodule
```

ports

Module

Module I/Os

Wire, reg
declarations

Concurrent
assignments

Procedural block

Sensitivity list

Sequential
statements

End module