
 


Need of FSM

 - Any digital design consists of two parts:
 - Data part :
 - Responsible for the processing of data.
 - The processing is done through some blocks such as (full adder, digital filter, decoder,...)
 - Control part
 - Describes how and when these blocks will communicate with each other.
 - Control part is generally described using a FSM(Finite State Machine).



Moore state Machine




Features:


- State machine outputs are dependent only on the present state
- Output vector (Y) is function of the state vector (S)
- Outputs don't react immediately to input change.

Advantage:

 - Moore machines effectively filter out transients.
- It can be used to eliminate race conditions when inputs are unfiltered.



Sequence-11

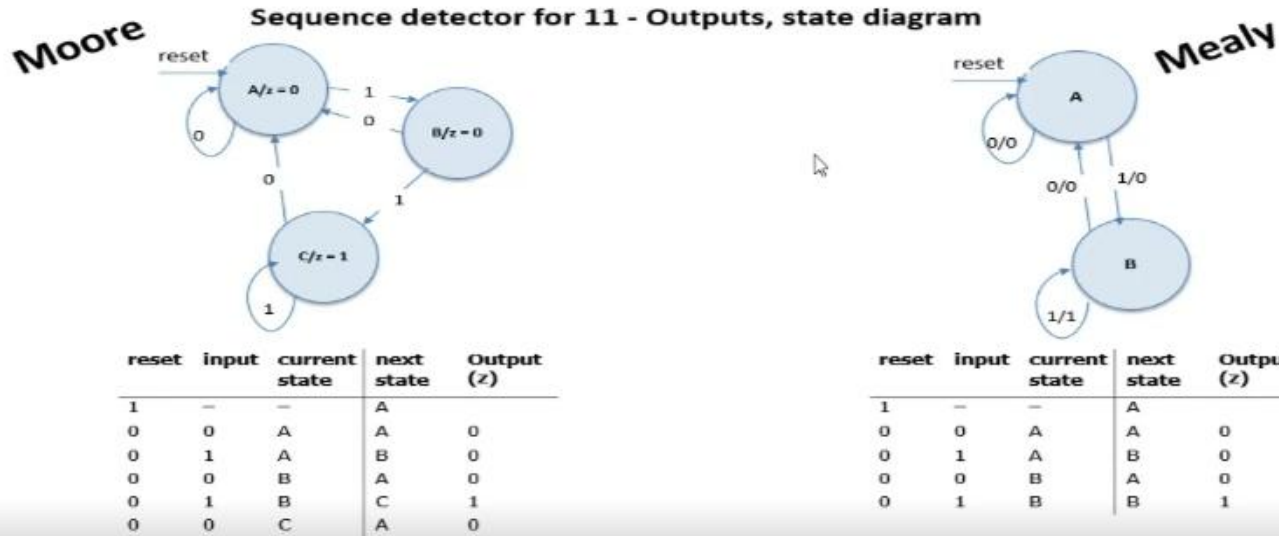

Moore Sequential Machine

```
module state_machine_moore(clk, reset, in, out);
```

```
parameter zero=0, one1=1, two1s=2;
```

```
output out; input clk, reset, in;
```

```
reg out; reg [1:0] state, next_state;
```

```
// Implement the state register
```

```
always @(posedge clk or posedge reset) begin
```

```
  if (reset)
```

```
    state <= zero;
```

```
  else
```


```
    state <= next_state;
```

```
  end
```

```
always @(state or in) begin
```

```
  case (state)
```
 
```
    zero: begin //last input was a zero out = 0;
```



```
if (reset)
    state <= zero;
else
    state <= next_state;
end

always @(state or in) begin
    case (state)
        zero: begin //last input was a zero out = 0;
            if (in)
                next_state=one1;
            else
                next_state=zero;
            end
        one1: begin //we've seen one 1 out = 0;
            if (in)
                next_state=two1s;
```

```
    next_state=zero;
  endcase
end
// output logic
always @(state) begin
  case (state)
    zero: out <= 0;
    one1: out <= 0;
    two1s: out <= 1;
    default: out <= 0;
  endcase
end
endmodule
```

Test Bench

```
`timescale 1ns/1ps

`include "state_machine_moore.v"

module state_machine_moore tb;

    reg clk, reset, in;

    wire out;

    // instantiate state machine

    state_machine_moore DUT (clk, reset, in, out);

    initial

        forever #5 clk = ~clk;
```

```
initial begin
```

```
    reset = 1'b1;
```

```
    clk = 1'b0;
```

```
    in = 0;
```

```
    #6;
```

```
    reset = 1'b0;
```

```
    for (j=0; j< 10; j=j+1) begin
```

```
        @(negedge clk); #1;
```

```
        in = $random;
```

```
        if (out == 1'b1)
```

```
            $display ("PASS : Sequence 11 detected \n");
```

```
        end
```

```
    #50;
```

```
    $finish;
```



```

reset = 1'b1;

clk = 1'b0;

in = 0;

#6;

reset = 1'b0;

for (j=0; j< 10; j=i+1) begin

    @(negedge clk); #1;
    in = $random;

    if (out == 1'b1)

        $display ("PASS : Sequence 11 detected \n");

    end

    #50;

    $finish;

end

endmodule

```

Test Bench

```
`timescale 1ns/1ps

`include "state_machine_moore.v"

module state_machine_moore tb;

    reg clk, reset, in;

    wire out;

    // instantiate state machine

    state_machine_moore DUT (clk, reset, in, out);

    initial

        forever #5 clk = ~clk;
```

```
initial begin
```

```
    reset = 1'b1;
```

```
    clk = 1'b0;
```

```
    in = 0;
```

```
    #6;
```

```
    reset = 1'b0;
```

```
    for (i=0; i< 10; i=i+1) begin
```

```
        I @(negedge clk); #1;
```

```
        in = $random;
```

```
        if (out == 1'b1)
```

```
            $display ("PASS; Sequence 11 detected \n");
```

```
        end
```

```
    #50;
```

```
    $finish;
```

```

reset = 1'b1;

clk = 1'b0;

in = 0;

#6;

reset = 1'b0;

for (j=0; j< 10; j=j+1) begin

    @(negedge clk); #1;
    in = $random;

    if (out == 1'b1)

        $display ("PASS : Sequence 11 detected \n");

    end

    #50;

    $finish;

end

endmodule

```

```


end
endmodule
//Test Bench
`timescale 1ns/1ps
`include "state_machine_moore.v"
module state_machine_moore_tb ;
    reg clk, reset, in;
    wire out;
    integer i;

    // instantiate state machine
    state_machine_moore DUT (clk, reset, in, out);
    initial
        forever #5 clk = ~clk;

    initial begin
        reset = 1'b1;
        clk = 1'b0;
        in = 0;
        #6;
        reset = 1'b0;

        for ( i=0; i< 10; i=i+1)
        begin
            @(negedge clk): #1;
            in = $random;
            if (out == 1'b1)
                $display ("PASS : Sequence 11 detected \n");
            end
            #50;
            $finish;
        end
    end
endmodule


```

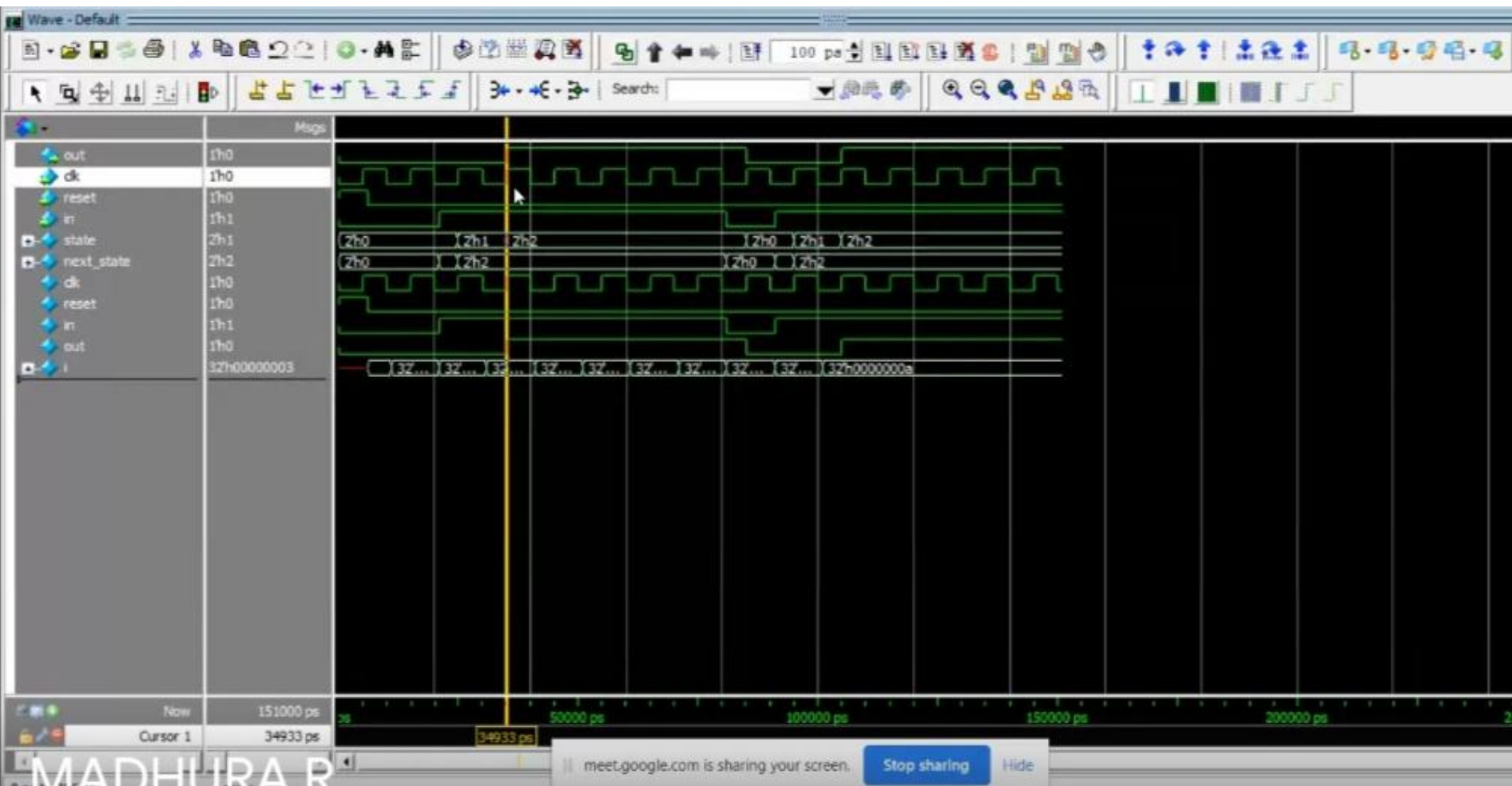

MADHURA R

Mealy state Machine

```
module state_machine_mealy (clk, reset, in, out);  
  input clk, reset, in;  
  output out;  
  reg out, state, next_state;  
  parameter zero=0, one=1;  
  //implement the state register  
  always@(posedge clk, posedge reset) begin  
    if (reset)  
      state <= zero;  
    else  
      state <= next_state;  
  end  
  always @(in or state)  
  
  case (state)  
    zero: begin  
      // last input was a zero  
      out=0;  
      if (in)  
        next_state  
      else
```

 


```

input clk, reset, in;
output out;
reg out, state, next_state;
parameter zero=0, one=1;
//Implement the state register
always@(posedge clk, posedge reset) begin
    if (reset)
        state <= zero;
    else
        state <= next_state;
End
always @(in or state)

case (state)
zero: begin
    //last input was a zero
    out=0;
    if (in)
        next_state = one;
    else
        next_state = zero;

```

 


```

forever #5 clk = ~clk;

initial begin
    reset = 1'b1;
    clk = 1'b0;
    in = 0;
    #6;
    reset = 1'b0;
    for (integer i=0; i< 10; i=i+1) begin
        @(negedge clk); #1;
        in = $random;
        if (out == 1'b1)
            $display ("PASS: Sequence 11 detected i=%d\n", i);
        end
        #50;
        $finish;
    end
end

```

