


Modeling Flip-Flops Using Always Block

a. Verilog Code for Simple Flip Flop

 b. Verilog code for Transparent Latch



```
always @ (posedge CLK)
begin
    Q <= D;
end
```




```
always @ (G or D)
begin
    if (G)
        Q <= D;
end
```



You



 Verilog code for DFF with Asynchronous clear



```
always @ (posedge CLK or negedge ClrN)
begin
    if (~ClrN)
        Q <= 0;
    else
        Q <= D;
end
```



You



Basic form of if

```
if (condition)
    sequential statements1
else
    sequential statements2
```

The condition is a Boolean expression that evaluates to TRUE or FALSE. If it is TRUE, sequential statements1 are executed; otherwise, sequential statements2 are executed.

Verilog **if** statements are sequential statements that can be used within an always block (or an initial block), but they cannot be used as concurrent statements outside of an always block. The most general form of the **if** statement is


```
if (condition)
    sequential statements
    // 0 or more else if clauses may be included
else if (condition)
    sequential statements}
[else sequential statements]
```



You



Nested if else loop

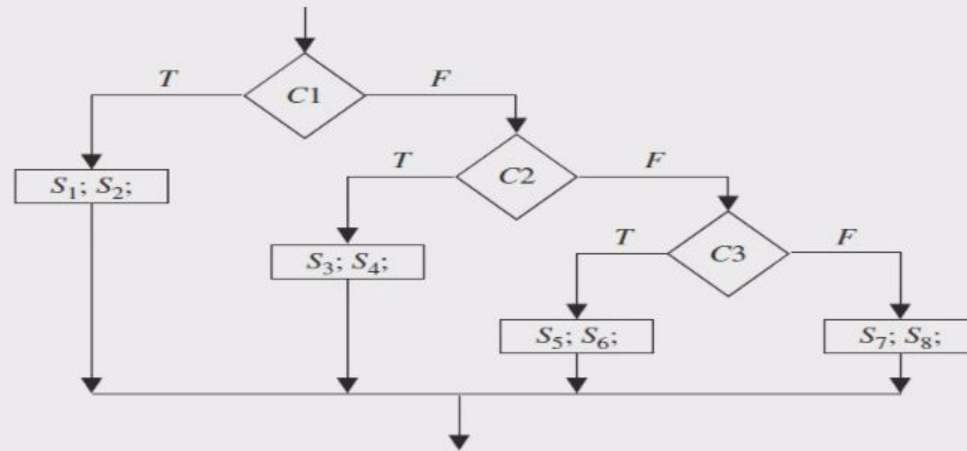


```
if (C1)
begin
    S1; S2;
end
else if (C2)
begin
    S3; S4;
end
else if (C3)
begin
    S5; S6;
end
else
begin
    S7; S8;
end
```



You



JK Flip Flop Verilog Code

 

```
module JKFF (SN, RN, J, K, CLK, Q, QN);  
  input SN, RN, J, K, CLK;  
  output Q, QN;  
  
  reg Qint;  
  
  always @(negedge CLK or RN or SN)  
  begin  
    if (~RN)  
      #8 Qint <= 0; // statement1  
    else if (~SN)  
      #8 Qint <= 1; // statement2  
    else  
      Qint <= #10 ((J && ~Qint) || (~K && Qint)); // statement3  
  end  
  
  assign Q = Qint; // statement4  
  assign QN = ~Qint; // statement5  
  
endmodule
```



You

