

Represent the decimal values 5, -2, 14, -10, 26, -19, 51, -43 as signed 7 bit numbers in the following formats

- 1) Sign magnitude
- 2) 1's complement
- 3) 2's complement

	Sign- magnitude	1's complement	2's complement
5	0,000101	0,000101	0,000101
-2	1,000010	1,111101	1,111110
14	0,001110	0,001110	0,001110
-10	1,001010	1110101	1110110
26	0011010	0011010	0011010
-19	1010011	1101100	1101101
51	0110011	0110011	0110011
-43	1101011	1010100	1010101



You're presenting to everyone  
Click here to return to the video call  
when you're ready to stop  
presenting  
Google Chrome • meet.google.com

10:39  
26-09-2020

## COMPUTER ORGANIZATION

### ADDITION & SUBTRACTION OF SIGNED NUMBERS

#### n-BIT RIPPLE CARRY ADDER

- A cascaded connection of  $n$  full-adder blocks can be used to add 2-bit numbers.
- Since carries must propagate (or ripple) through cascade, the configuration is called an  $n$ -bit ripple carry adder (Figure 9.1).

$x_i$	$y_i$	Carry-in $c_i$	Sum $s_i$	Carry-out $c_{i+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i = \bar{x}_i \bar{y}_i c_i + \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + x_i y_i c_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = y_i c_i + x_i c_i + x_i y_i$$

Example:

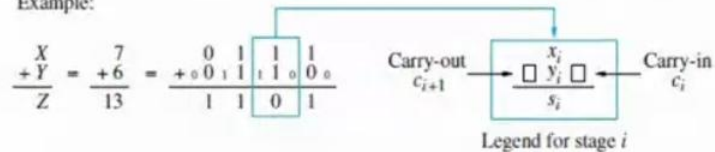



Figure 9.1 Logic specification for a stage of binary addition.




You




### COMPUTER ORGANIZATION

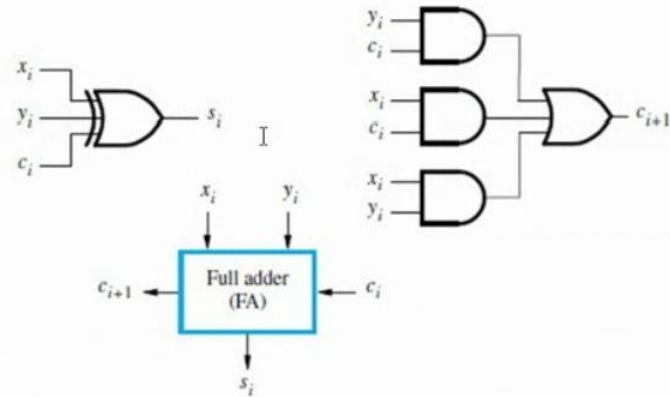


(a) Logic for a single stage

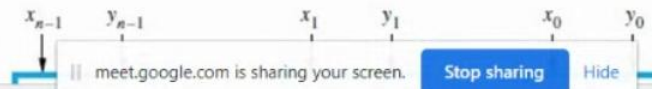


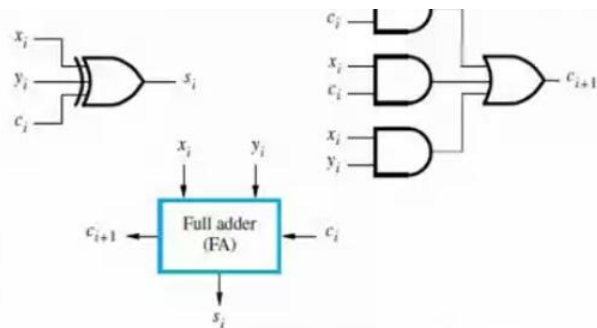

(a) Logic for a single stage

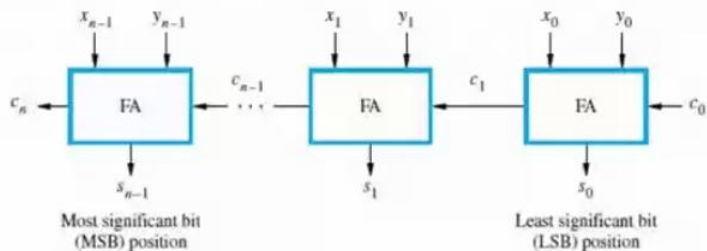

(b) An  $n$ -bit ripple-carry adder

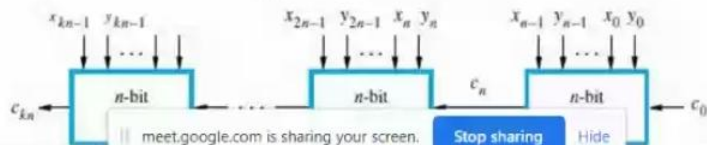

meet.google.com is sharing your screen.

Stop sharing

Hide

You



## COMPUTER ORGANIZATION

### ADDITION/SUBTRACTION LOGIC UNIT

- The  $n$ -bit adder can be used to add 2's complement numbers  $X$  and  $Y$  (Figure 9.3).
- **Overflow** can only occur when the signs of the 2 operands are the same.
- In order to perform the subtraction operation  $X - Y$  on 2's complement numbers  $X$  and  $Y$ ; we form the 2's complement of  $Y$  and add it to  $X$ .
- Addition or subtraction operation is done based on value applied to the Add/Sub input control-line.
- Control-line=0 for addition, applying the  $Y$  vector unchanged to one of the adder inputs.
- Control-line=1 for subtraction, the  $Y$  vector is 2's complemented.

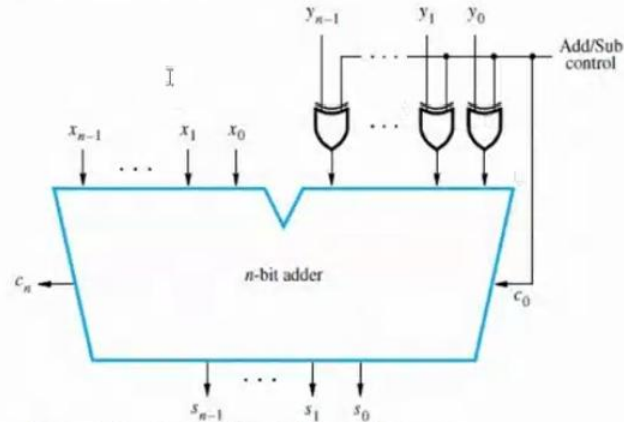


Figure 9.3 Binary addition/subtraction logic circuit.

