

$$x(n) = \{1, 2, 3, 4\} \quad h(n) = \{1, -1, -1\}$$

$$L = N_1 + N_2 - 1 = 4 + 2 - 1 = 5$$

$$y(n) = \{1, -1, -3, -5, -7, -4\}$$

1	-1	-1
2	-2	-2
3	-3	-3
4	-4	-4

Using DFT

$$Y(n) = \{5(n) + 2\delta(n-1) + 3\delta(n-2) + 4\delta(n-3)\}^*$$

Using FFT

$$N=2$$

$$x(n) = \{1, 2, 3, 4, 0, 0, 0, 0\}$$


$$h(n) = \{1, -1, -1, 0, 0, 0, 0, 0\}$$

$$Y(k) = X(k) \cdot H(k)$$

Activate Window  
Go to Settings to activate

MOZHIS

## 4-bit carry-lookahead Adder

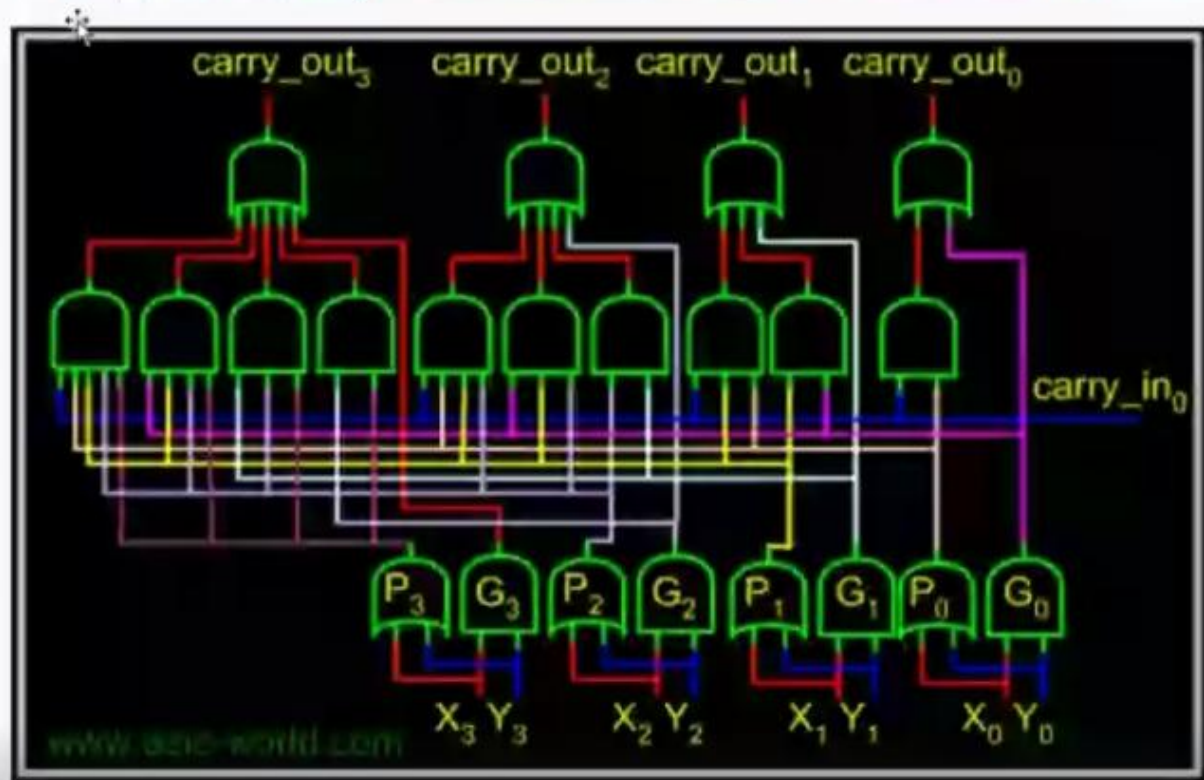

# Multiplication of unsigned numbers

$$\begin{array}{r} \phantom{000} 1\ 1\ 0\ 1 \quad (13) \text{ Multiplicand } M \\ \phantom{000} 1\ 0\ 1\ 1 \quad (11) \text{ Multiplier } Q \\ \hline \phantom{000} 1\ 1\ 0\ 1 \\ \phantom{000} 1\ 1\ 0\ 1 \\ \phantom{000} 0\ 0\ 0\ 0 \\ \phantom{000} 1\ 1\ 0\ 1 \\ \hline 1\ 0\ 0\ 0\ 1\ 1\ 1\ 1 \quad (143) \text{ Product } P \end{array}$$

**Product of 2  $n$ -bit numbers is at most a  $2n$ -bit number.**


**Unsigned multiplication can be viewed as addition of shifted versions of the multiplicand.**

## Multiplication of unsigned numbers (contd..)

- We added the partial products at end.
  - Alternative would be to add the partial products at each stage.
- Rules to implement multiplication are:
  - If the  $i^{\text{th}}$  bit of the multiplier is 1, shift the multiplicand and add the shifted multiplicand to the current value of the partial product.
  - Hand over the partial product to the next stage
  - Value of the partial product at the start stage is 0.


# Multiplication of unsigned numbers

Typical multiplication cell

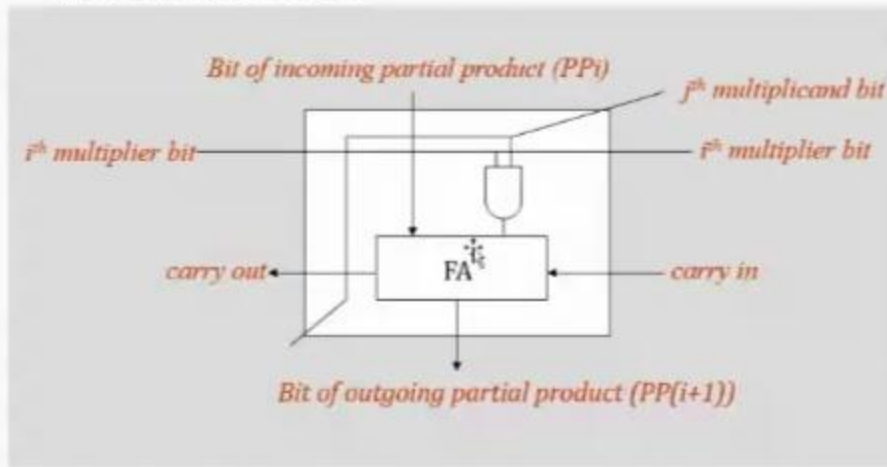

# Combinatorial array multiplier


Combinatorial array multiplier

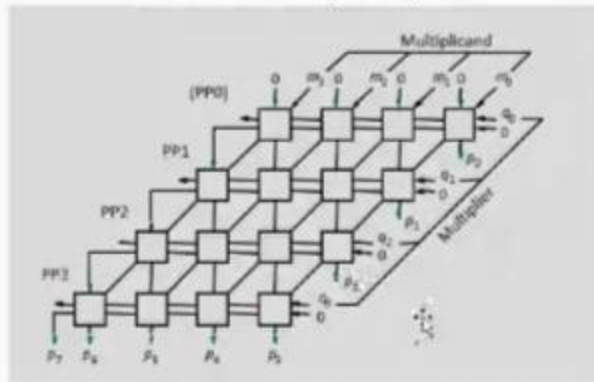

Product is:  $p_3p_2p_1p_0$

Multiplicand is shifted by displacing it through an array of adders.

## Sequential Circuit Multiplier

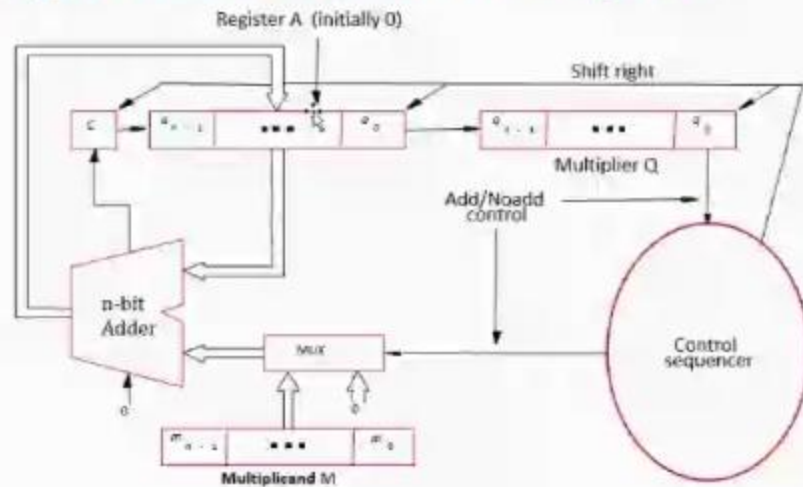


LSB OF Q-0 NO ADD SIGNAL IS  
GENERATED

LSB OF Q-1 ADD SIGNAL IS  
GENERATED



## Sequential multiplication (contd..)

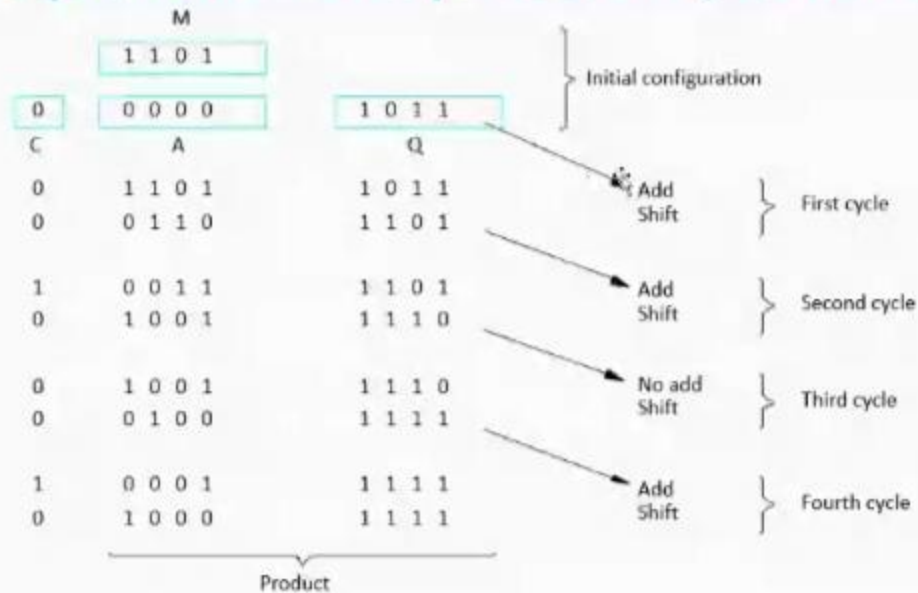

## Booth Algorithm

- Since  $0011110 = 0100000 - 0000010$ , if we use the expression to the right, what will happen?

[illegible]